

FACHGESPRACH – 16

DDC CONTROLLER DIGITAL OUTPUTS

WTF Philosophy:

If you don't remember a certain formula,
That's OK - you can always `GoogleTheShit`.
But bad engineering CONCEPTS costs the
Company money.

WTF Institute Mission:

Teach correct engineering CONCEPTS to our
PEs and PMs.


DIGITAL OUTPUT

- ➡ A Digital Output is a controller output that is either ON or OFF – nothing in between (sometimes called a Binary Output by snootholes who have taken some Boolean Algebra in college)
- ➡ BUT
- ➡ If that's all there is to it – you could all go home now and not have to sit through some very convoluted shit for the next 45 minutes


WHAT IS THE PURPOSE OF THIS DISCUSSION?

- ➡ Not Electronics Technology
- ➡ "Layout-Awareness" is my goal
- ➡ The slides that follow will show what that means
- ➡ And please be patient. The slides may appear to be randomly arranged – but it will all come together

Every DO **MUST** Form This Simple Loop

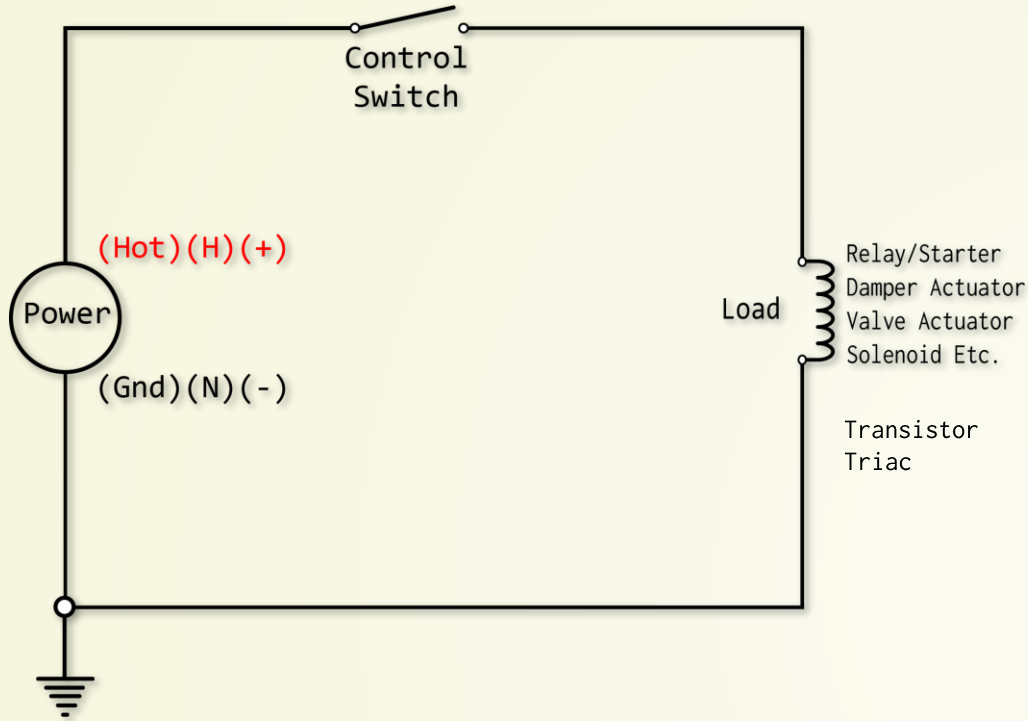

Equivalent Circuit

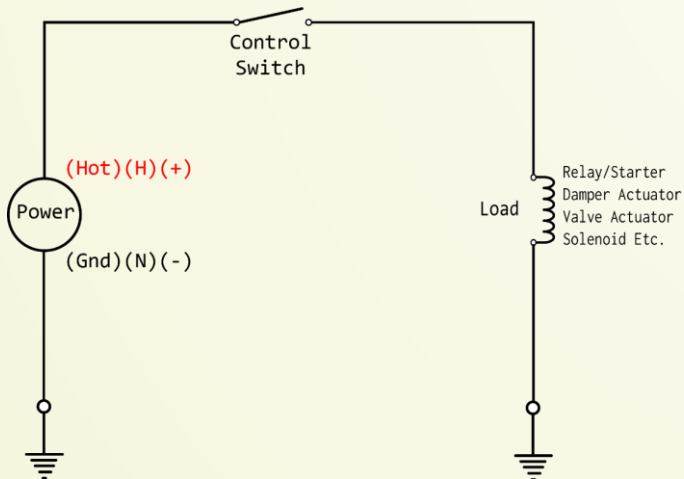

12 Question Checklist – For Good Design

LOAD:

1. What Voltage level/type does it require?
2. How many Amps does it draw? Or VA?

POWER:

3. Where is this Power coming from (Next Slide)?
(Only 1 power source in one loop.)
4. Type AC or DC - does it match LOAD?
5. Voltage Level – does it match LOAD?
6. Power source VA sufficient for LOAD?
7. What if there are multiple LOADS?


CONTROL SWITCH:

8. Where is it located in the circuit? (May not be as shown on sketch.)
9. What are the Switch Amp and Voltage rating?
10. Can it carry the LOAD Current and Voltage?

SURGE PROTECTION:

11. Required?
12. Built-in?

POWER SOURCE FOR DO

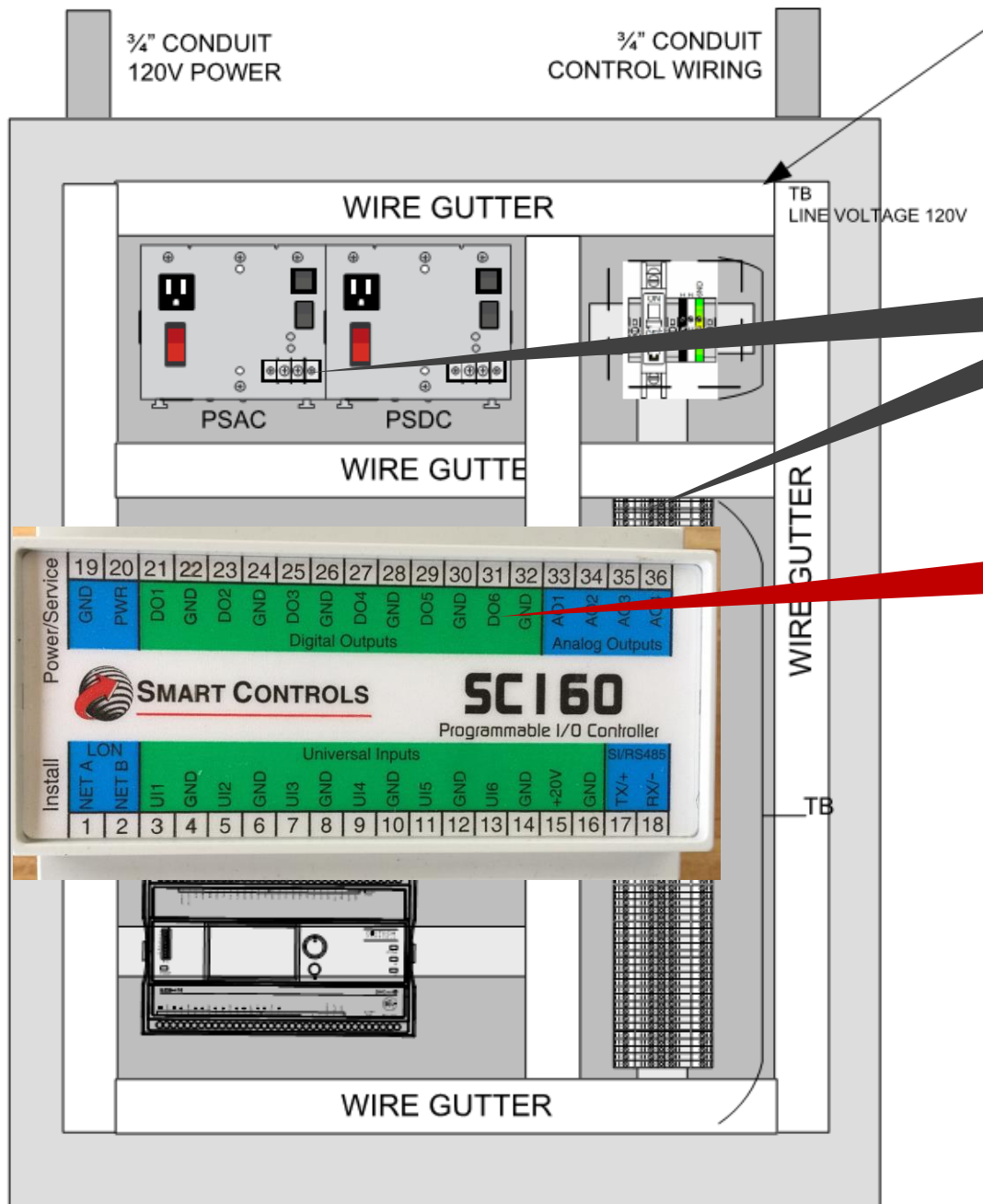


You can get 24Vac here (PS Terminal Block)

You can get 24Vac here (Sourcing Triacs)



V-dc usually sourced by controllers

Install new 24 Volt transformer in a box with 120 Volt power and disconnect switch

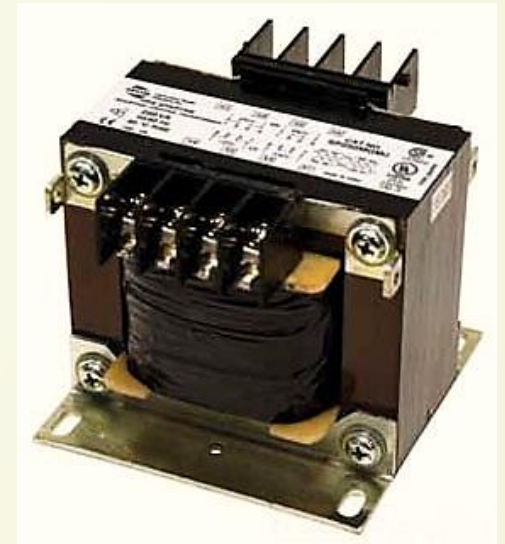There is usually a control transformer in the motor starter – if everything matches you can think about using that



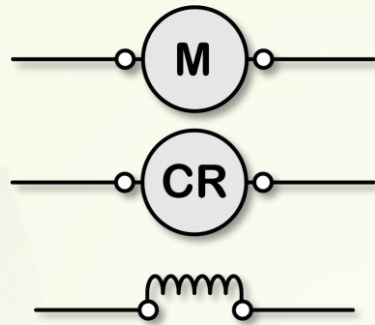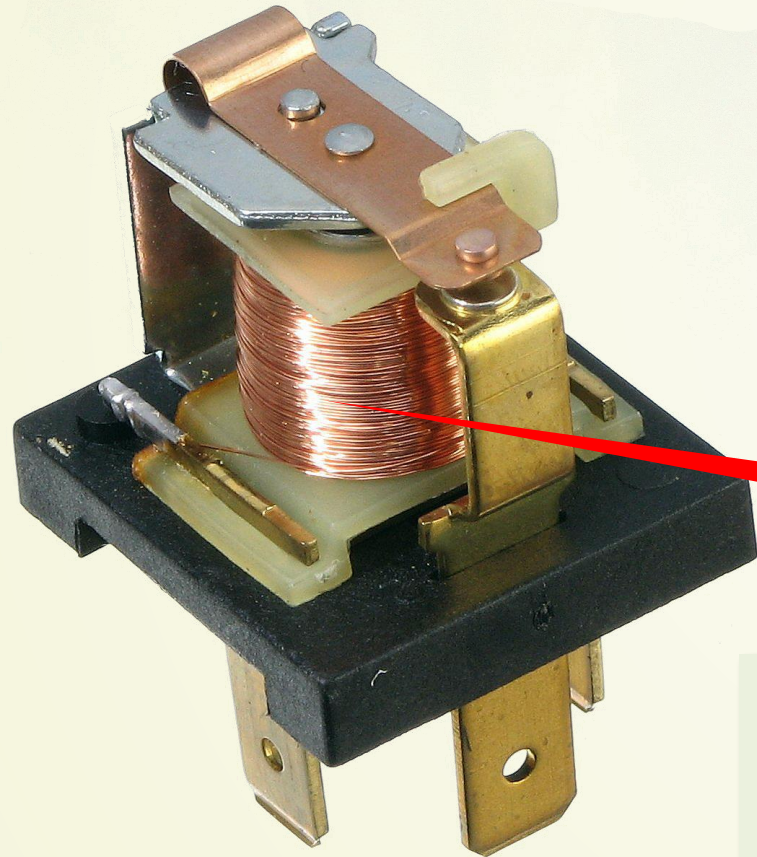THE MOST COMMON LOAD TYPE ON DIGITAL OUTPUTS



Relay Coil Symbols

To Power a coil you MUST KNOW:


- AC or DC
- Voltage
- Amp Draw
- AC Inrush
- Kick-back Protection

Relay Contacts Ratings and Transient Voltage Suppression will be our next discussion. So we will not discuss it today.

Relay
Coil

Remember: This coil is the "LOAD" on our Digital Output. A coil is an inductive load.

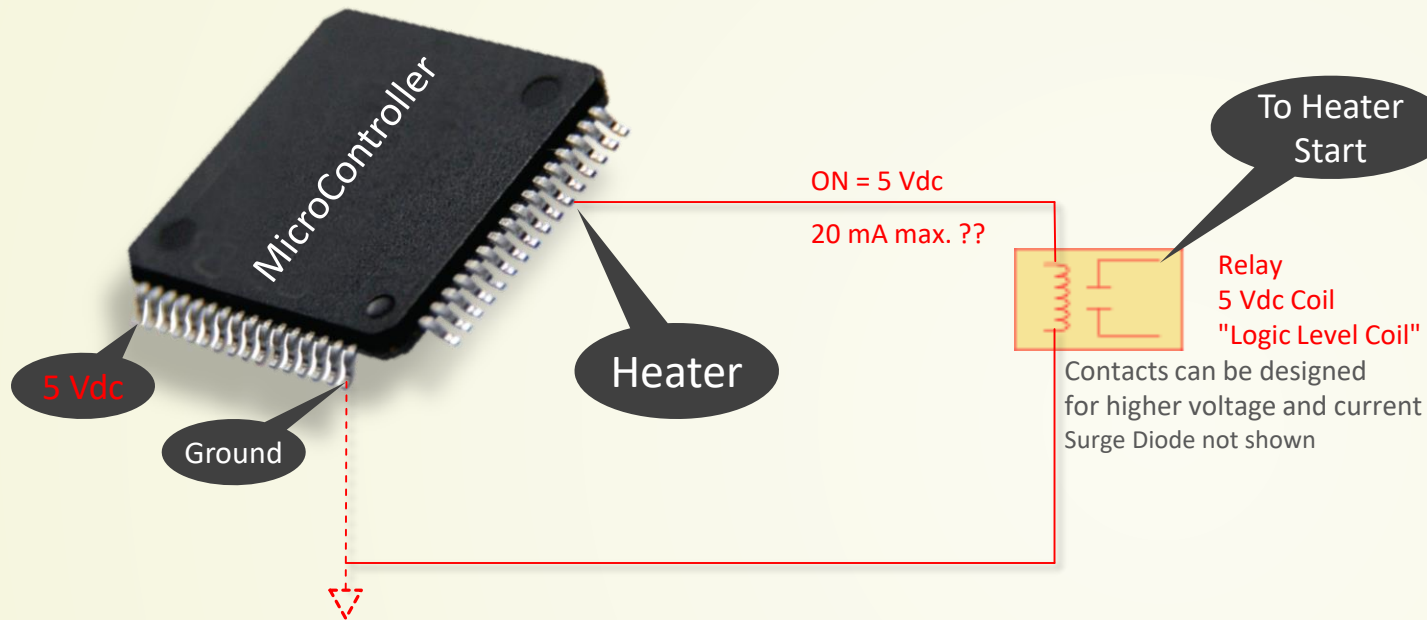AT THE VERY BOTTOM OF IT ALL – THIS HAPPENS



Pseudocode:


```
11 = heater;
```

```
If (RoomTemp < 70)
```

```
    io_out(heater, ON); //make this pin high or output 5 volts
```



```
Else if(RoomTemp > 73)
```
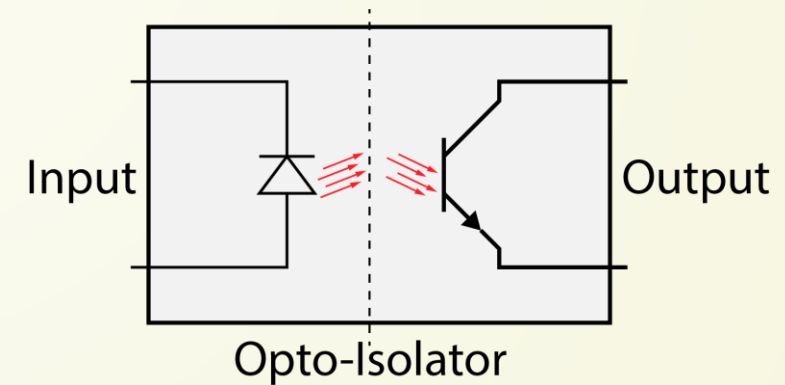
```
    io_out(heater, OFF); //make this pin low or output 0 volts
```




ELECTRONIC LEVERAGE

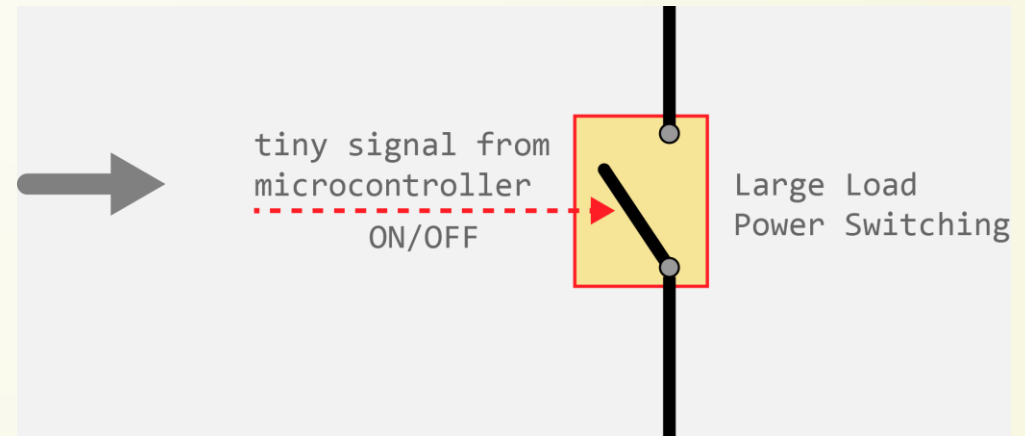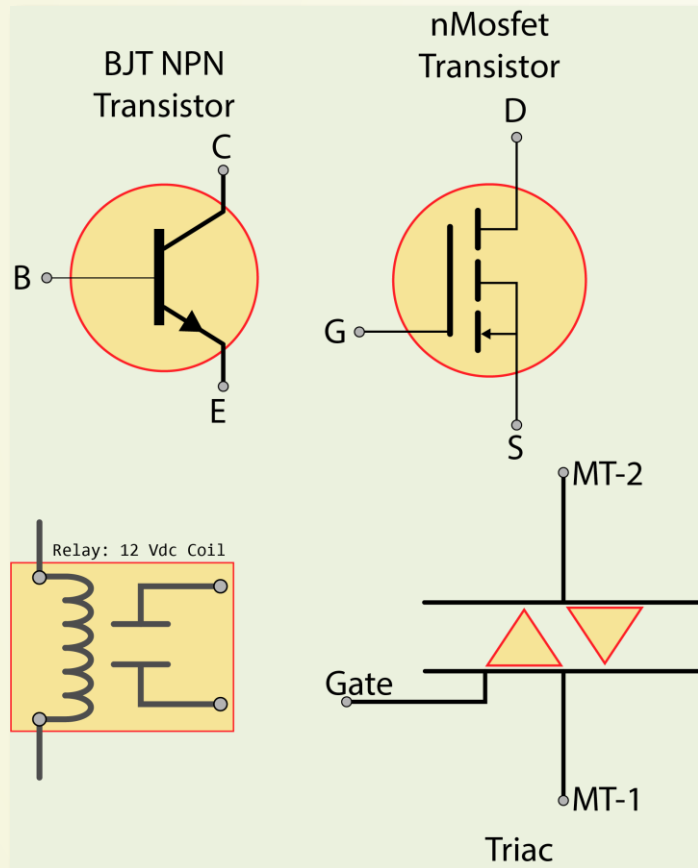- Small Current (Voltage) turning ON/OFF large Currents and higher Voltages.



ELECTRONIC LEVERAGE

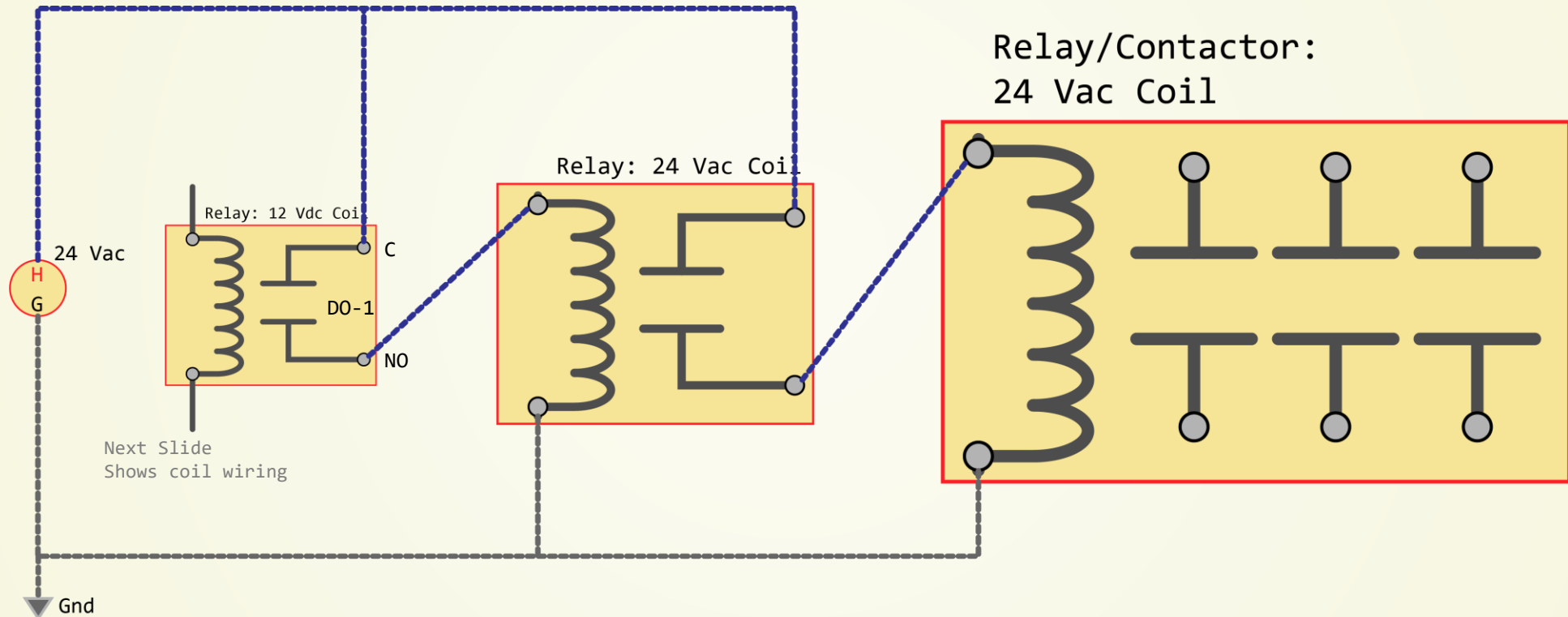
- Small Current (Voltage) turning ON/OFF large Currents and higher voltages.





Can we omit the middle
relay and go direct to
Starter?
Wait till later slides.

DIGITAL OUTPUT RELAY – DRY CONTACTS

HOW MICROCONTROLLERS TURN RELAYS ON/OFF

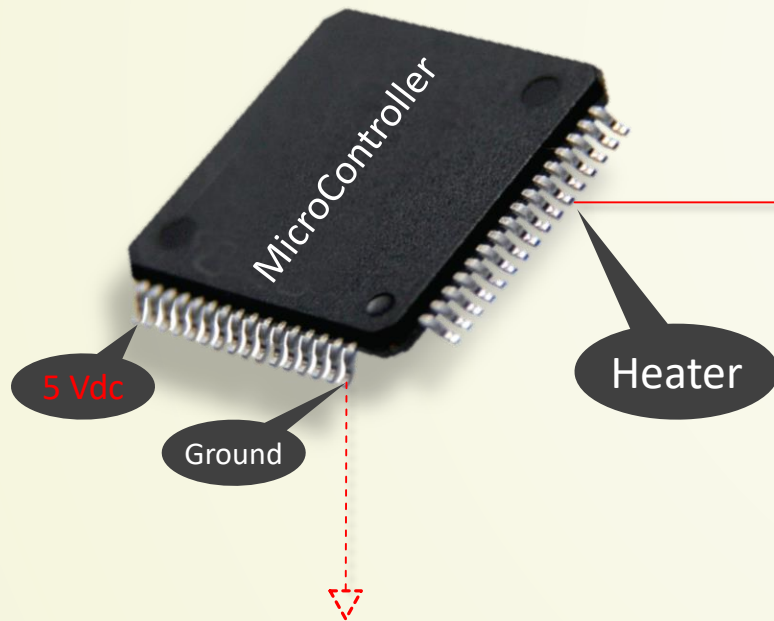

ON = 5 Vdc
20 mA max. ??

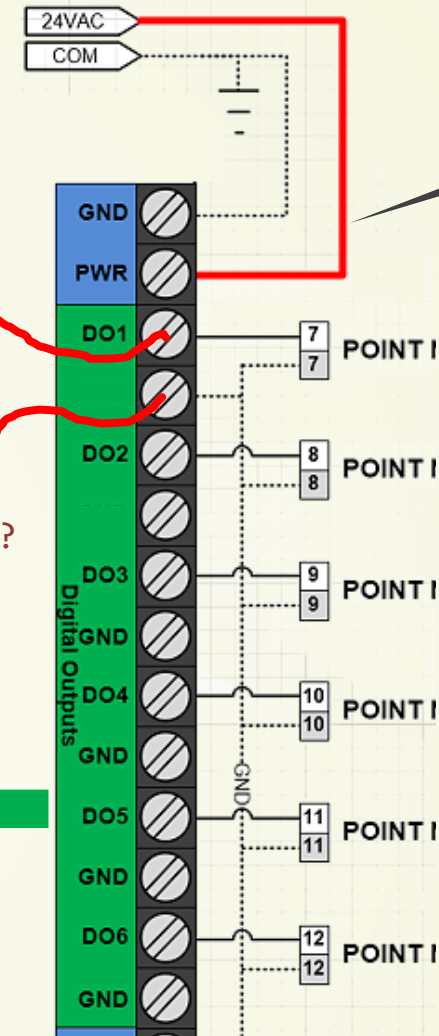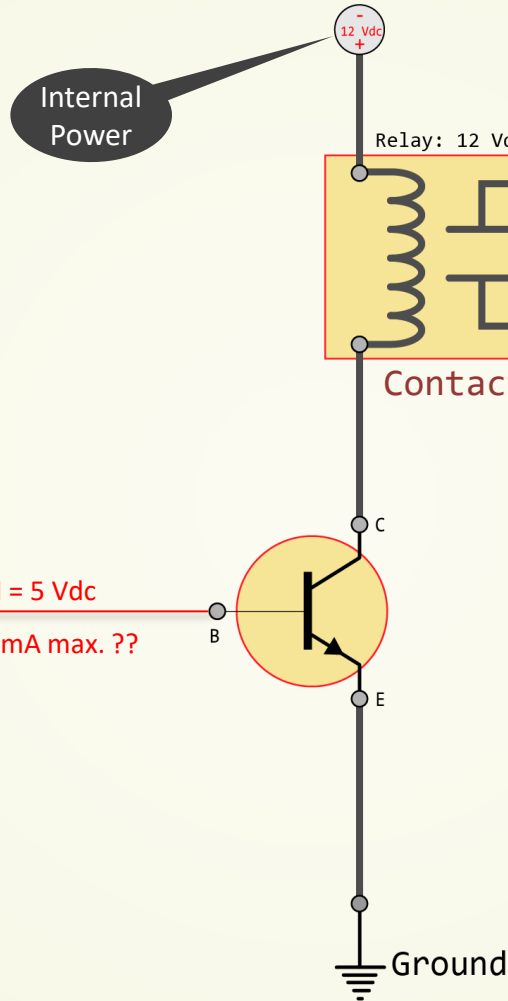


You can use this for
power or a separate one

Troubleshooting

Note:
Don't get hung up on the electronics here.
Not all components shown.

"LAYOUT-AWARENESS" – COMPONENT LOCATIONS

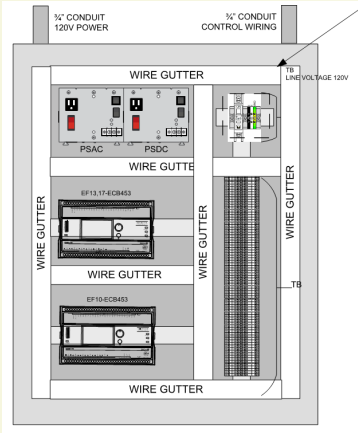

How Far?


WAC Supplied Control Panel

Locate Close to Input/Sensors




MCC by Electrical

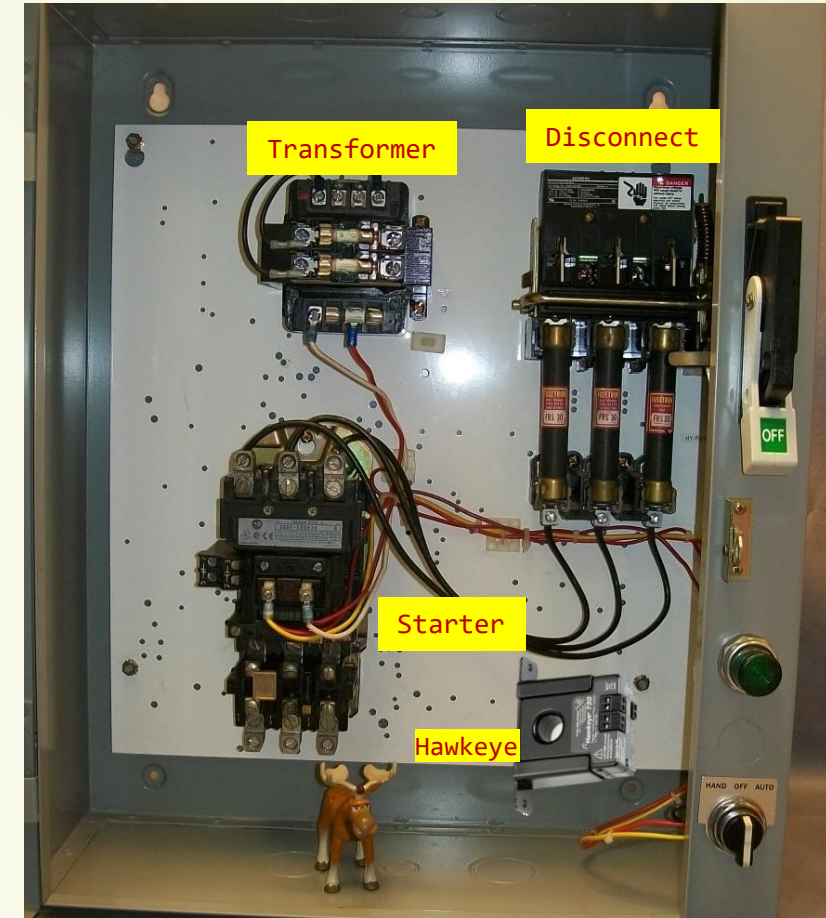Sometimes, the starters are free-standing, not in a MCC



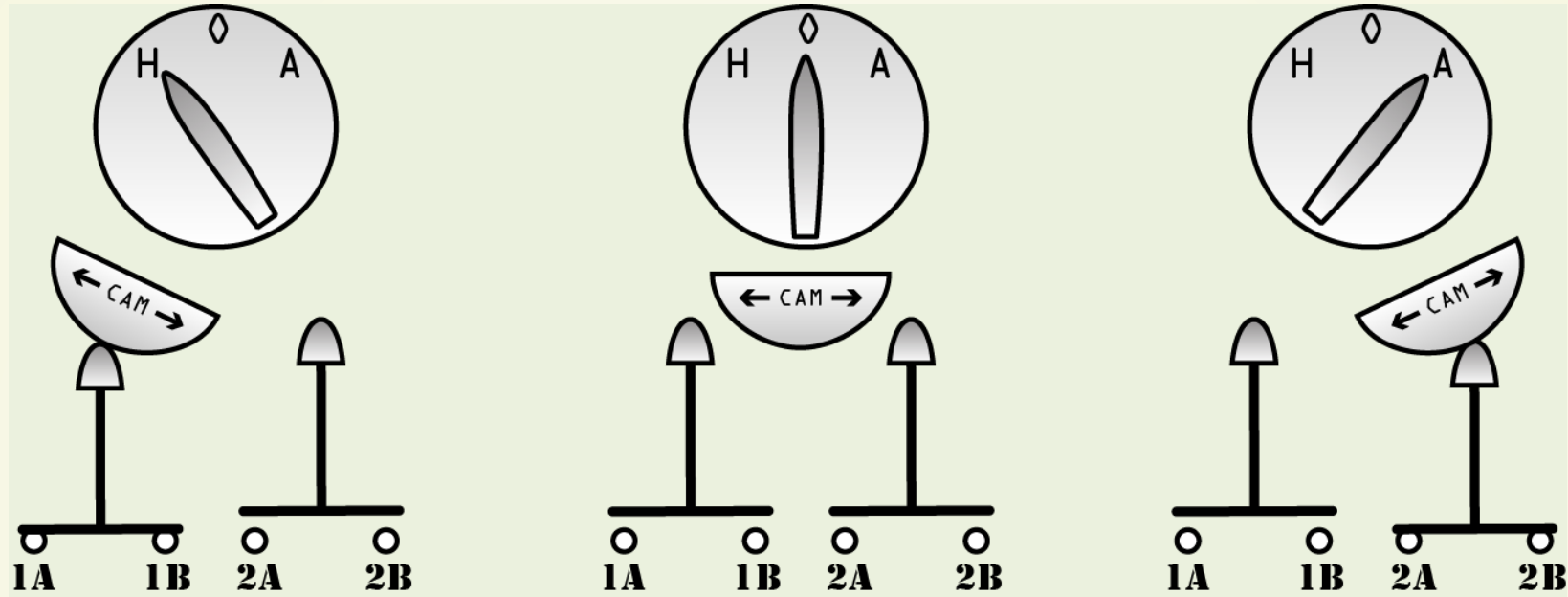Motor Starter and Disconnect in MCC
HOA Switch on Starter










CONTACT	H	O	A
1A - 1B	CLOSED	OPEN	OPEN
2A - 2B	OPEN	OPEN	CLOSED

- The H0A switch belongs to a general family of switches known as “Cam Operated Selector Switches”.
- H0A switches have only 2 contacts.
- Basically, a Selector Knob turns a Cam that pushes pins at different locations to make or break contacts.
- These contacts cannot be considered either NO or NC.

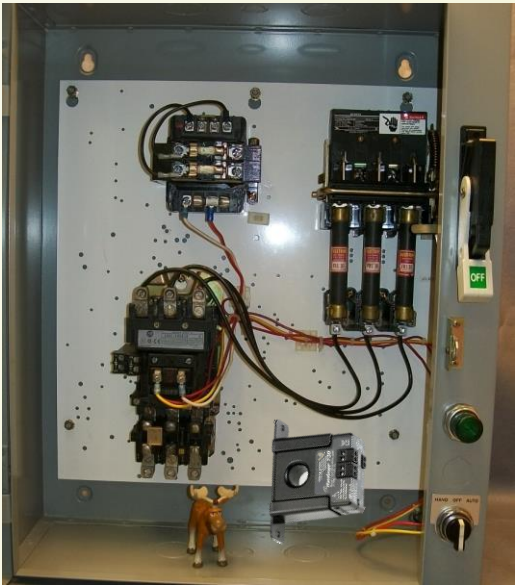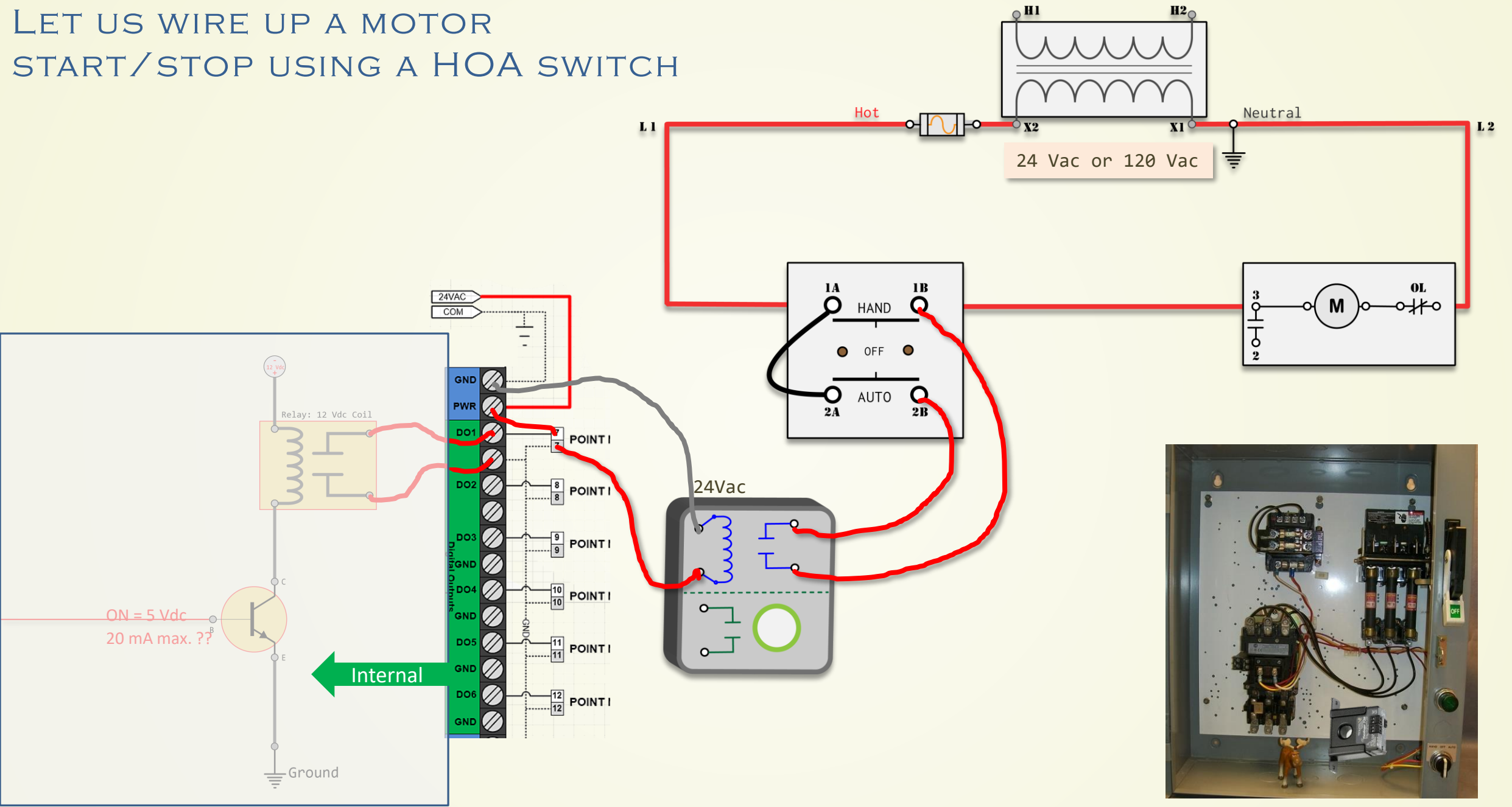LET US WIRE UP A MOTOR START/STOP USING A HOA SWITCH



DELETE THE PILOT (MIDDLE) RELAY?

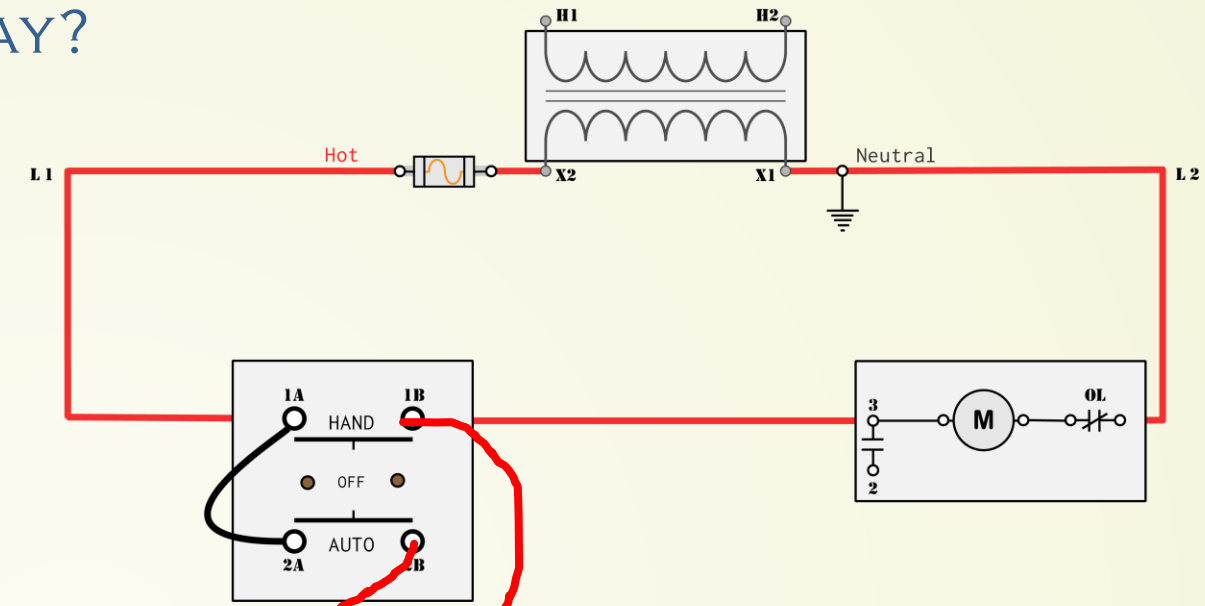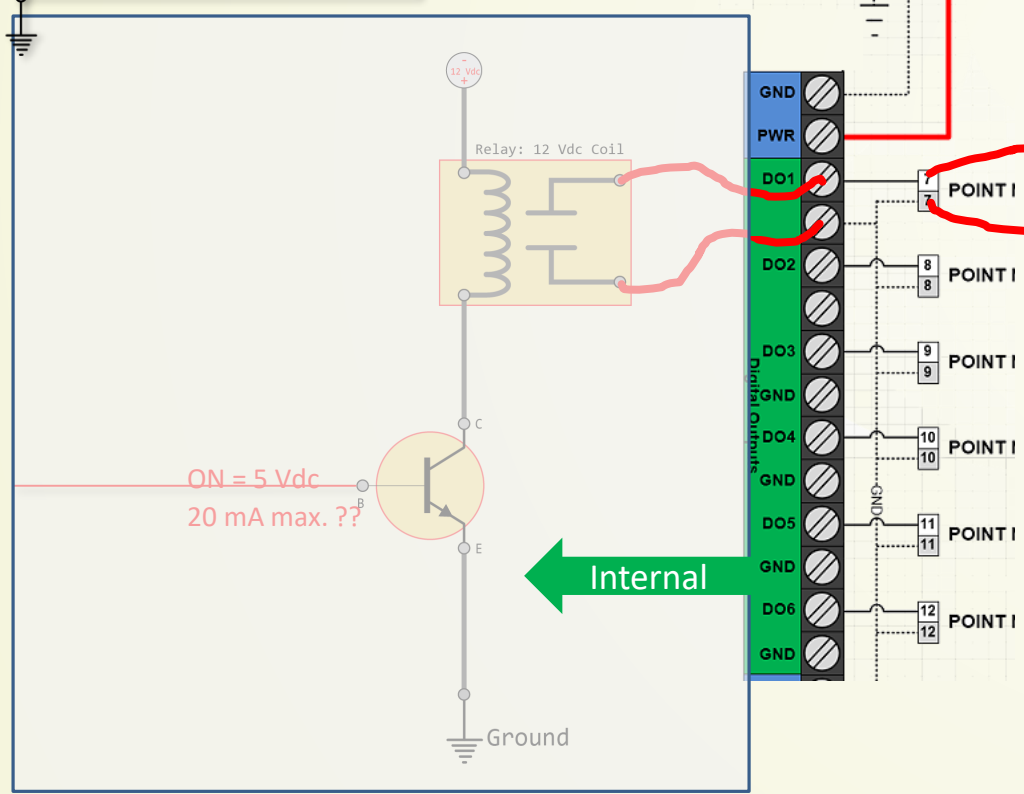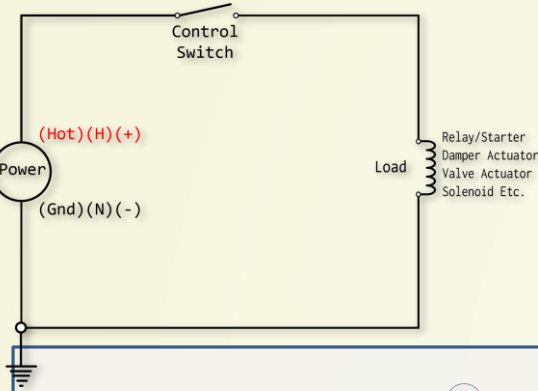


Starter Coil Load


Description	Contactor Catalog Number/Size		
	CN15A NEMA Size 00	CN15B NEMA Size 0	CN15D NEMA Size 1
Maximum Horsepower (hp)			
1-Phase 115V	1/3	1	2
230V	1	2	3
3-Phase 200V	1-1/2	3	7-1/2
230V	1-1/2	3	7-1/2
460V	2	5	10
575V	2	5	10
AC Magnet Coil Data			
Pick-Up Volts — Cold	74%	74%	74%
Pick-Up Volts — Hot	78%	78%	78%
Pick-Up Voltamperes	80	100	230
Pick-Up Watts	49	65	95
Sealed Voltamperes	7.5	10	28
Sealed Watts	2.4	3.1	7.8

NEVER MIX TRANSFORMER POWER

Control
Transformer #1

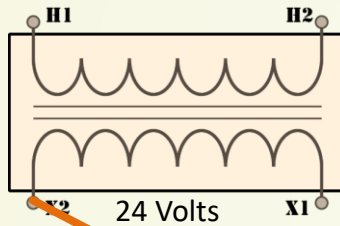

Control
Transformer #2

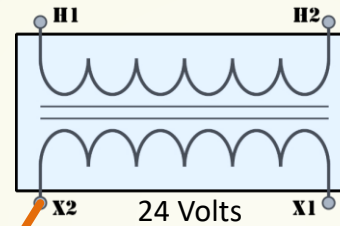

Never do this!


To parallel transformers you need to match both polarity and phase. If you inadvertently do as shown here – chances are very good that smoke will come out of the control panel.

SMART CONTROLS TRIAC OUTPUTS

PS
24VAC/100 VA
PSH100AB10

24VAC
COM

Inside the Smart Controls Unit

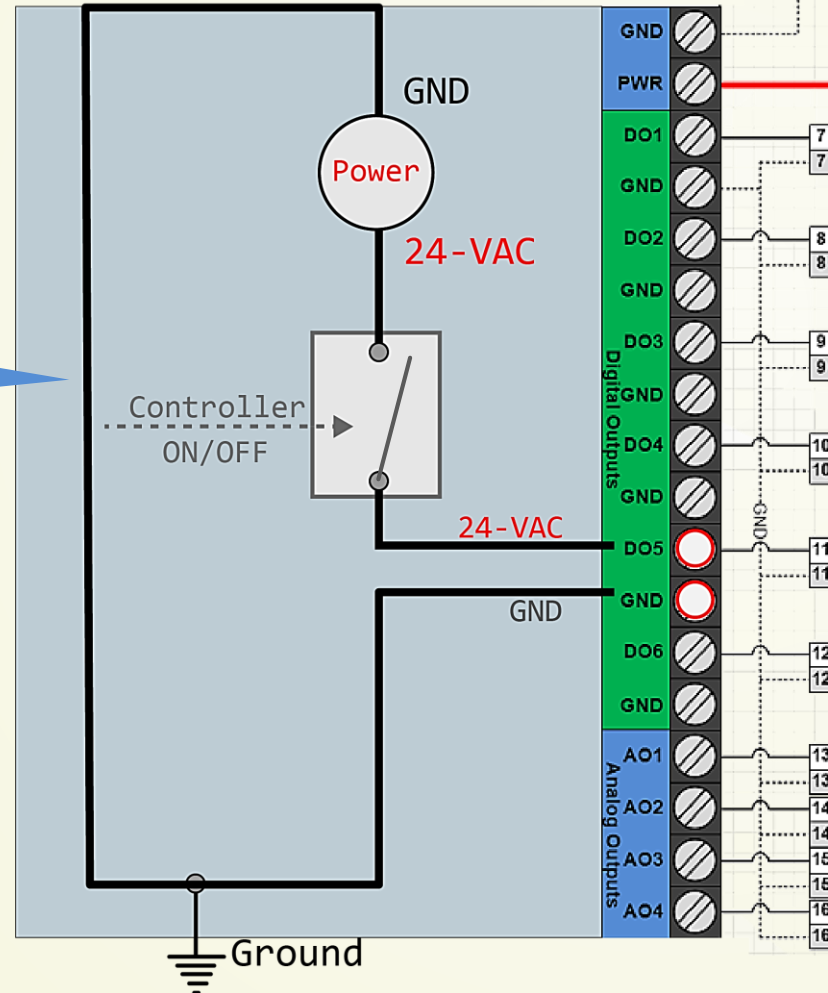


Outputs


Number: 10
6- Digital: Triac 1.0 A @ 24 VAC
Voltage Sourcing
4-Analog: 0-10V
Analog Resolution: 12 bit
Accuracy: $\pm 1\%FS$ (25°C, 77°F)
Protection Circuitry: ESD

Notes:
TVS not shown
How to troubleshoot?

WIRING SMART CONTROLS TRIAC OUTPUTS

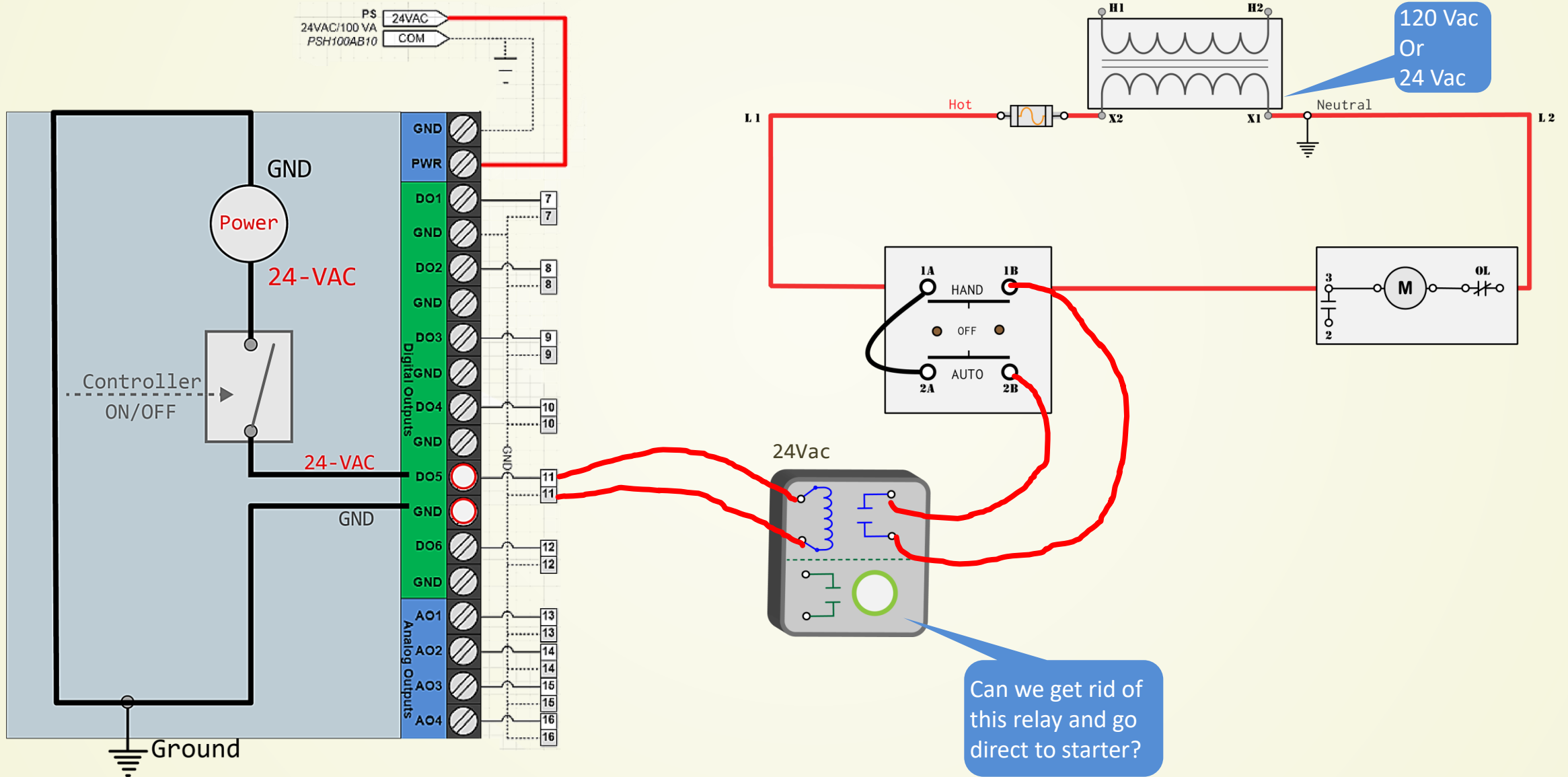

Distech Triac Output

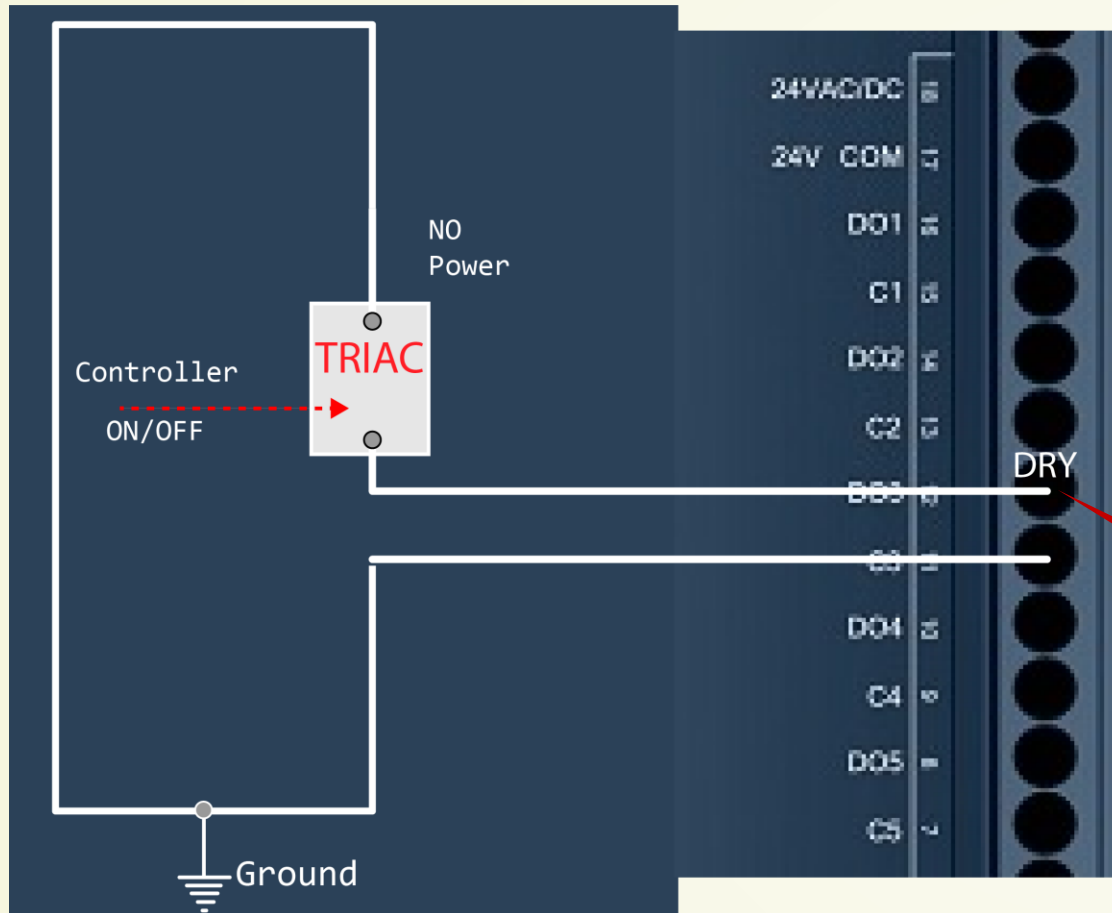

Wiring Triac Outputs

Digital outputs are all made of triacs and there is no voltage present on the output terminals. Therefore, an external power source has to be added if necessary.



To measure the state of a triac output, an external load must be connected.

Troubleshooting

Connect the digital output according to the following figure if a relay is being controlled.


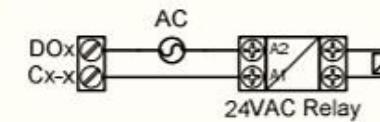


Figure 9-1: Digital triac output – Relay

Distech Discrete Output

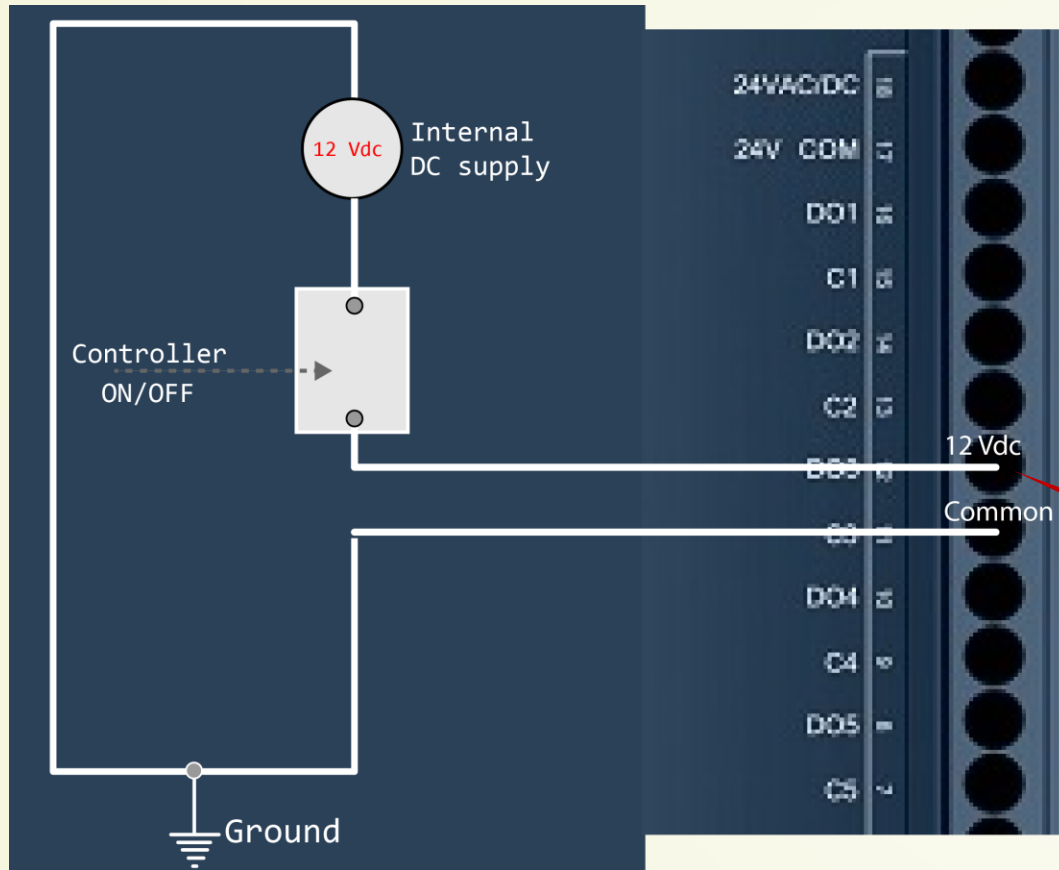

Wiring Universal Outputs

Universal outputs can be configured to provide either a discrete signal of 0 or 12VDC, a linear signal ranging from 0 to 10VDC or a 0 to 20mA signal (ECP-400 Series and ECP-500 Series). The discrete signal can be used to generate a pulse wave modulation (PWM) signal or a simple two-state signal. These outputs are protected by an auto-reset fuse.

Wiring Discrete Outputs

When controlling a relay with a universal output, a diode must be connected in parallel to protect the controller from back-emf current which occurs when the relay is turned off. It is recommended to use diodes that are part of the 1N400x family and they should be placed closer to the relay.


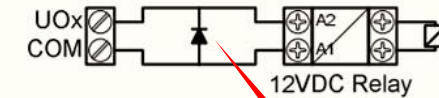


Figure 9-3: Discrete 0 or 12VDC universal output – Relay



Need a 12 Volt DC Coil Relay
(Powered by Controller)


12 Volt DC
Coil

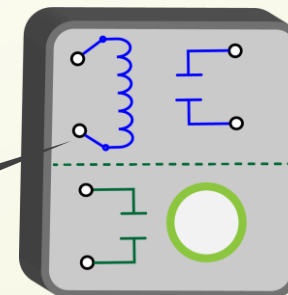

Troubleshooting

SOURCING VS SINKING OUTPUTS

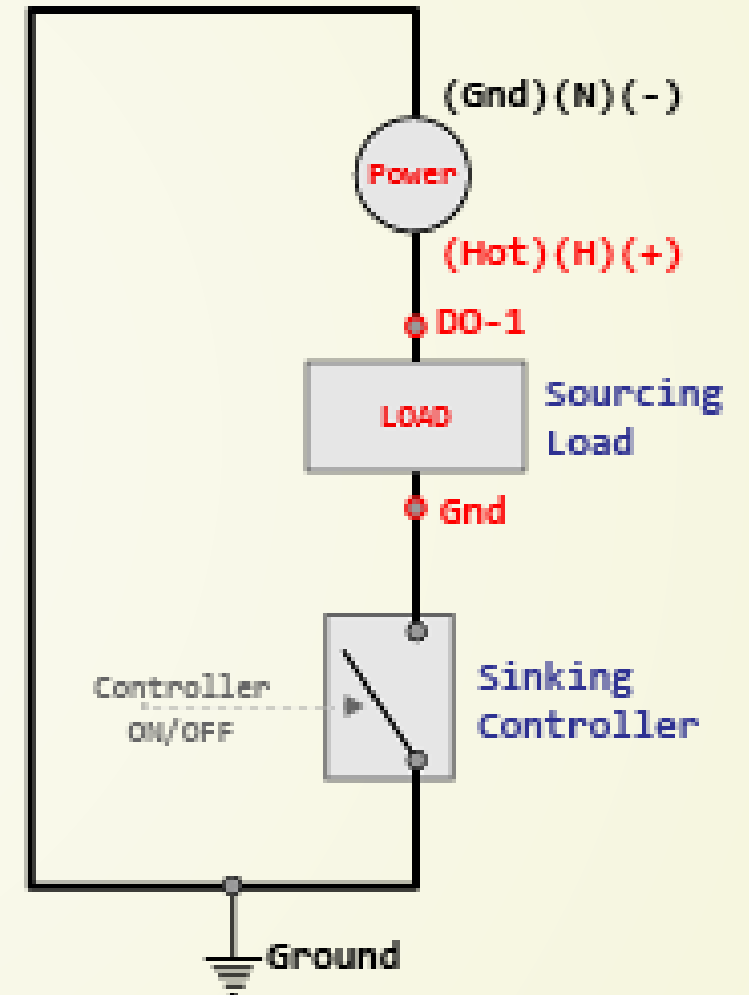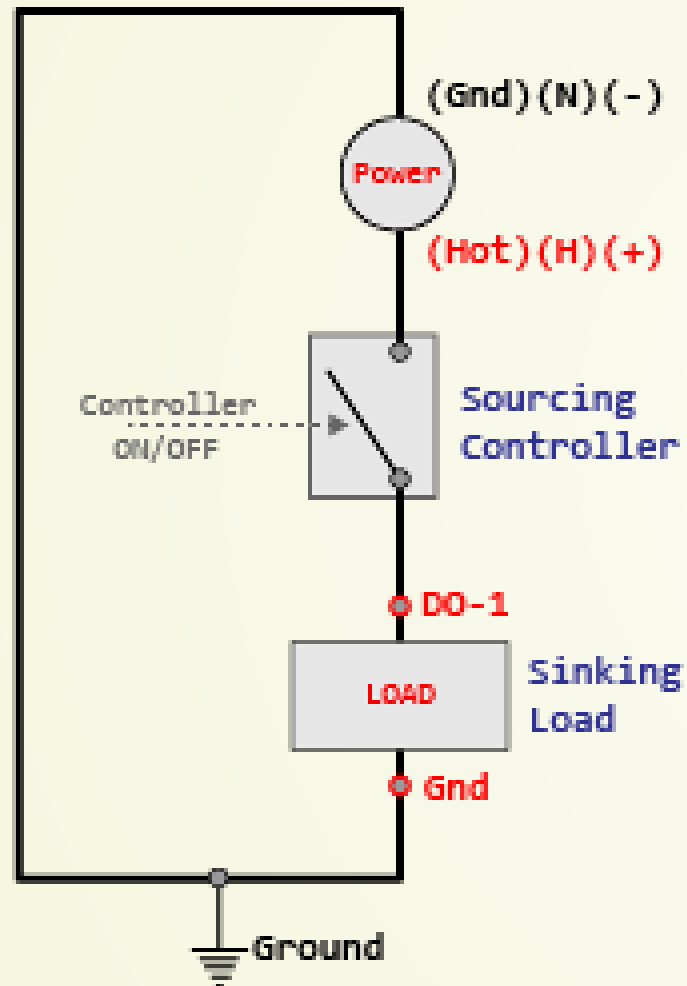

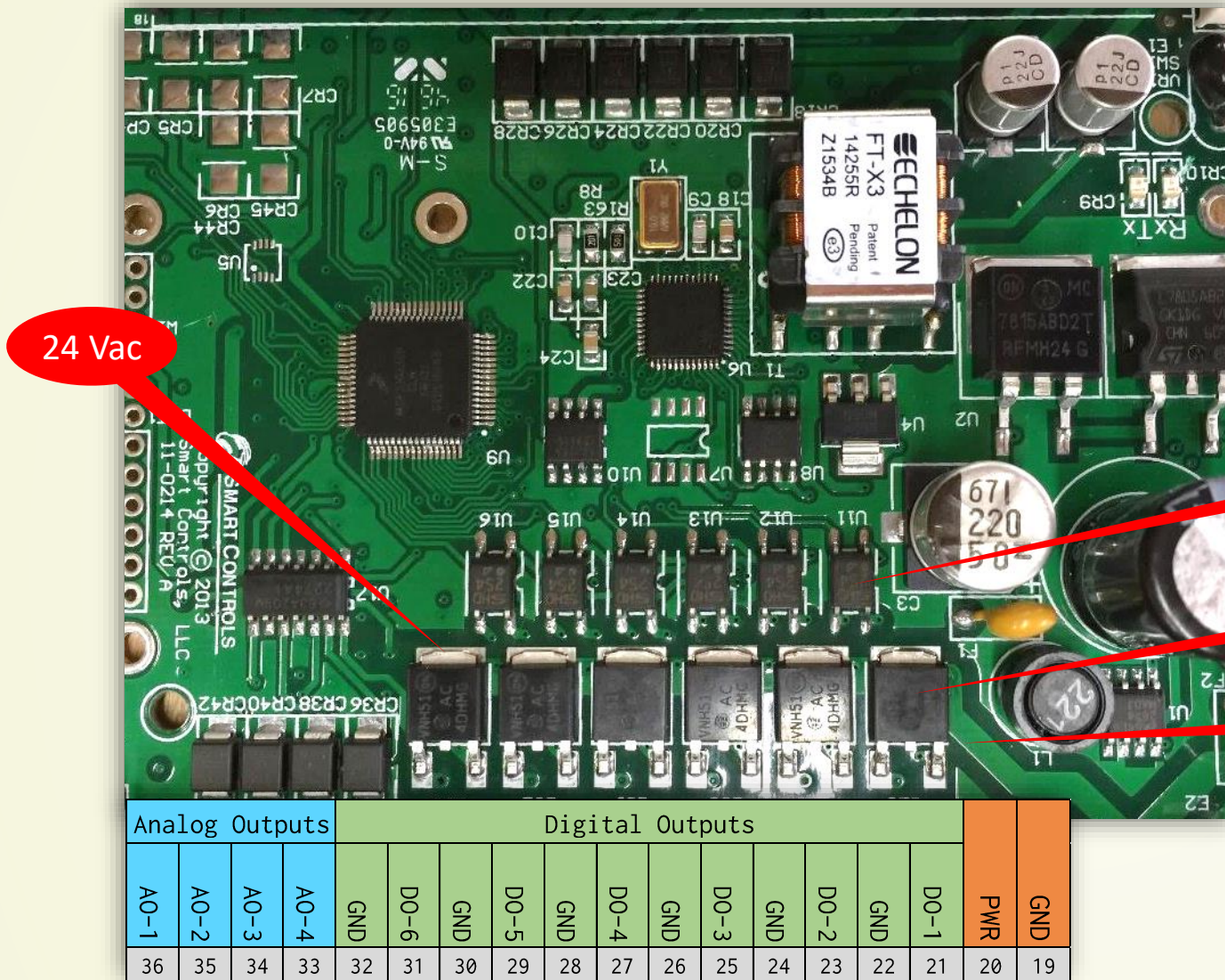


Outputs	
Number:	10
6- Digital:	Triac 1.0 A @ 24 VAC Voltage Sourcing
4-Analog:	0-10V
Analog Resolution:	12 bit
Accuracy:	±1%FS (25°C, 77°F)
Protection Circuitry:	ESD

Opto Coupler

Triac 1 Amp

TVS on back side

Smart Controls SC-160

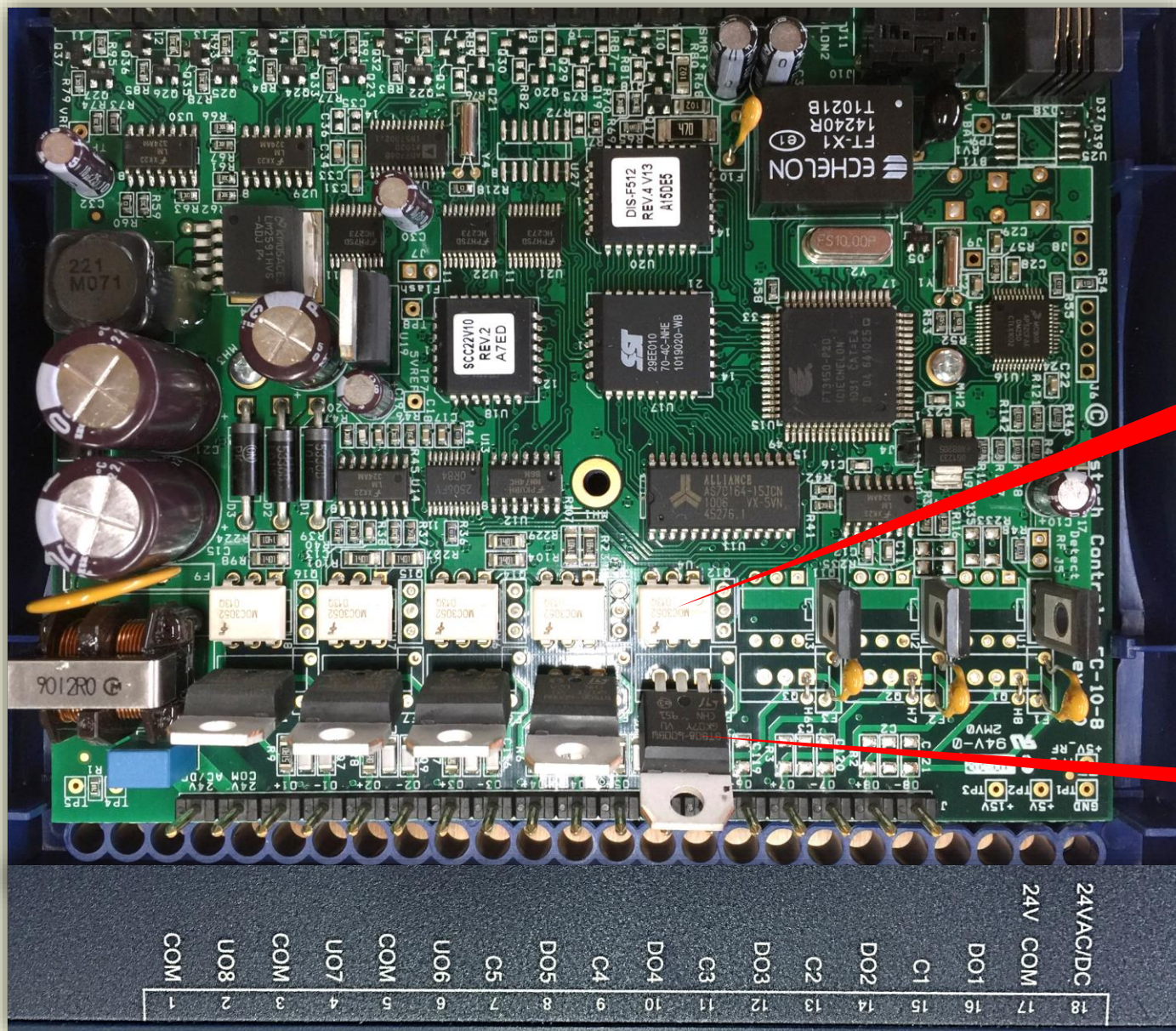

Outputs

Digital

- 24 VAC Triac, digital (on/off), PWM, or floating¹; software configurable
 - 0.5A continuous
 - 1.0A @ 15% duty cycle for a 10-minute period
 - PWM control: adjustable period from 2 seconds to 15 minutes
 - Floating control: requires two consecutive outputs¹
 - Min pulse on/off: 500msec.
 - Adjustable drive time period

External or internal power supply (jumper selectable)

Opto Coupler



life.augmented

BTA08, BTB08, T810, T835, T850

Snubberless™, logic level and standard 8 A Triacs

Triac
0.5 Amp

Distech ECP-203



NEXT DISCUSSION:

- TVS - TRANSIENT VOLTAGE SUPPRESSION
 - RELAY CONTACTS AND TRIAC RATINGS
 - CONTROL TRANSFORMER SIZING
- (ALL ABOVE ARE RELATED TOPICS)